 



 
TITLE PAGE

Class	:	BE - 8
Roll. No	:	42428
Assignment No.	:	A. 3
Assignment Name	:	FIFO
Date Of Performance	:	3-10-2020 to 10-10-2020

Block Diagram:



Truth-Table :

rst	clk	wr_en	data_out	full	empty
1	X	X	(00) ₁₆	0	1
0		0	N.A	0 -> 1	0
0		1	data_in	1	0

MAIN VHDL PROGRAM

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;

entity FIFO_4x8 is
    Port ( data_in : in  STD_LOGIC_VECTOR (7 downto 0);
          rst : in  STD_LOGIC;
          clk : in  STD_LOGIC;
          wr_en : in  STD_LOGIC;
          data_out : out STD_LOGIC_VECTOR (7 downto 0);
          empty : inout STD_LOGIC;
          full : inout STD_LOGIC);
end FIFO_4x8;

architecture FIFO_4x8_ARCH of FIFO_4x8 is
    TYPE MEMORY IS ARRAY(0 TO 3) OF STD_LOGIC_VECTOR(7 DOWNT0 0);
    SIGNAL MEM : MEMORY:={X"00",X"00",X"00",X"00"};
    SIGNAL FRONT : INTEGER:=0;
    SIGNAL REAR : INTEGER:=0;
begin
    PROCESS(data_in,rst,clk,wr_en,empty,full)
    BEGIN

        IF rst='1' THEN
            FRONT<=0;
            REAR<=0;
            data_out<=X"00";
            MEM<={X"00",X"00",X"00",X"00"};
            empty<='1';
            full<='0';
        ELSIF FALLING_EDGE(clk) THEN
            IF wr_en='0' THEN
                IF (REAR>3 OR full='1') THEN
```








```


        full<='1';
    ELSE
        MEM(REAR)<=data_in;
        REAR<=REAR+1;
        empty<='0';
        IF (REAR>=3) THEN
            full<='1';
        END IF;
    END IF;
ELSE
    IF (empty='1') THEN
        empty<='1';
    ELSIF (FRONT=3) THEN
        data_out<=MEM(FRONT);
    ELSE
        data_out<=MEM(FRONT);
        FRONT<=FRONT+1;
    END IF;
END IF;
END IF;

END PROCESS;
end FIFO_4x8_ARCH;


```


RTL SCHEMATIC

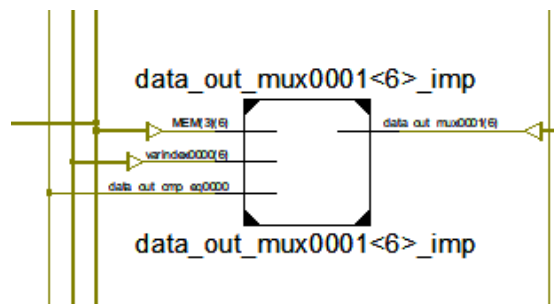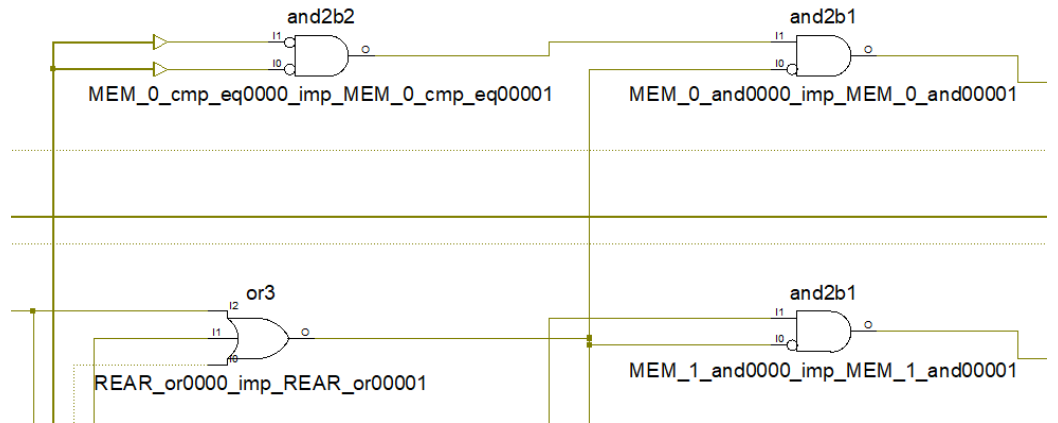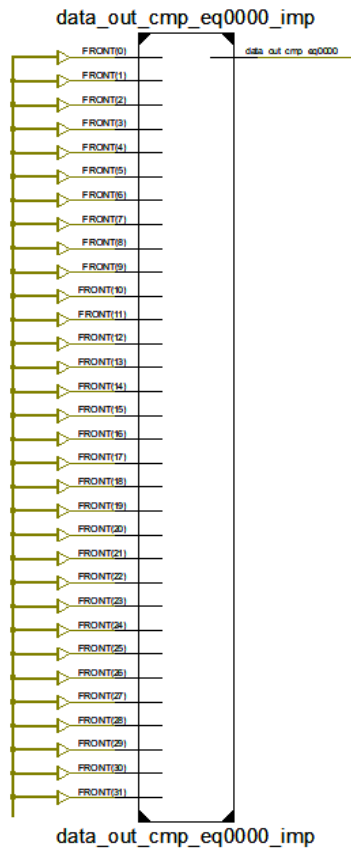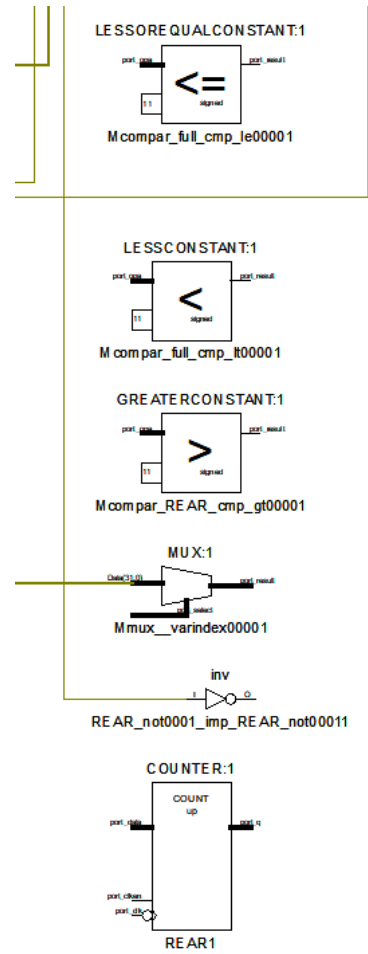  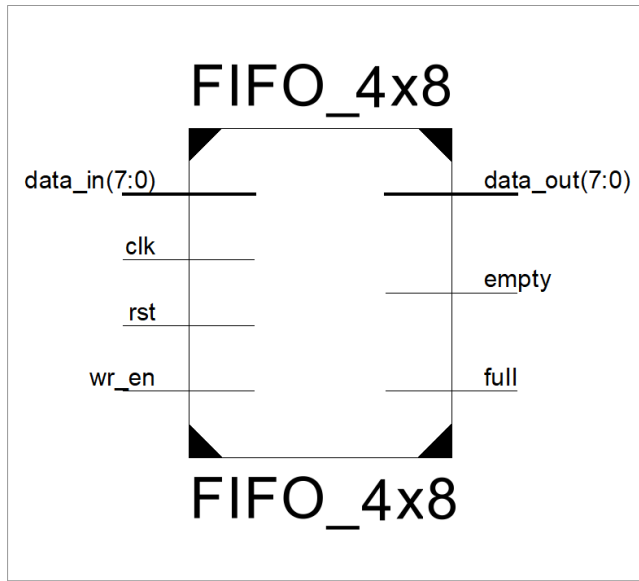

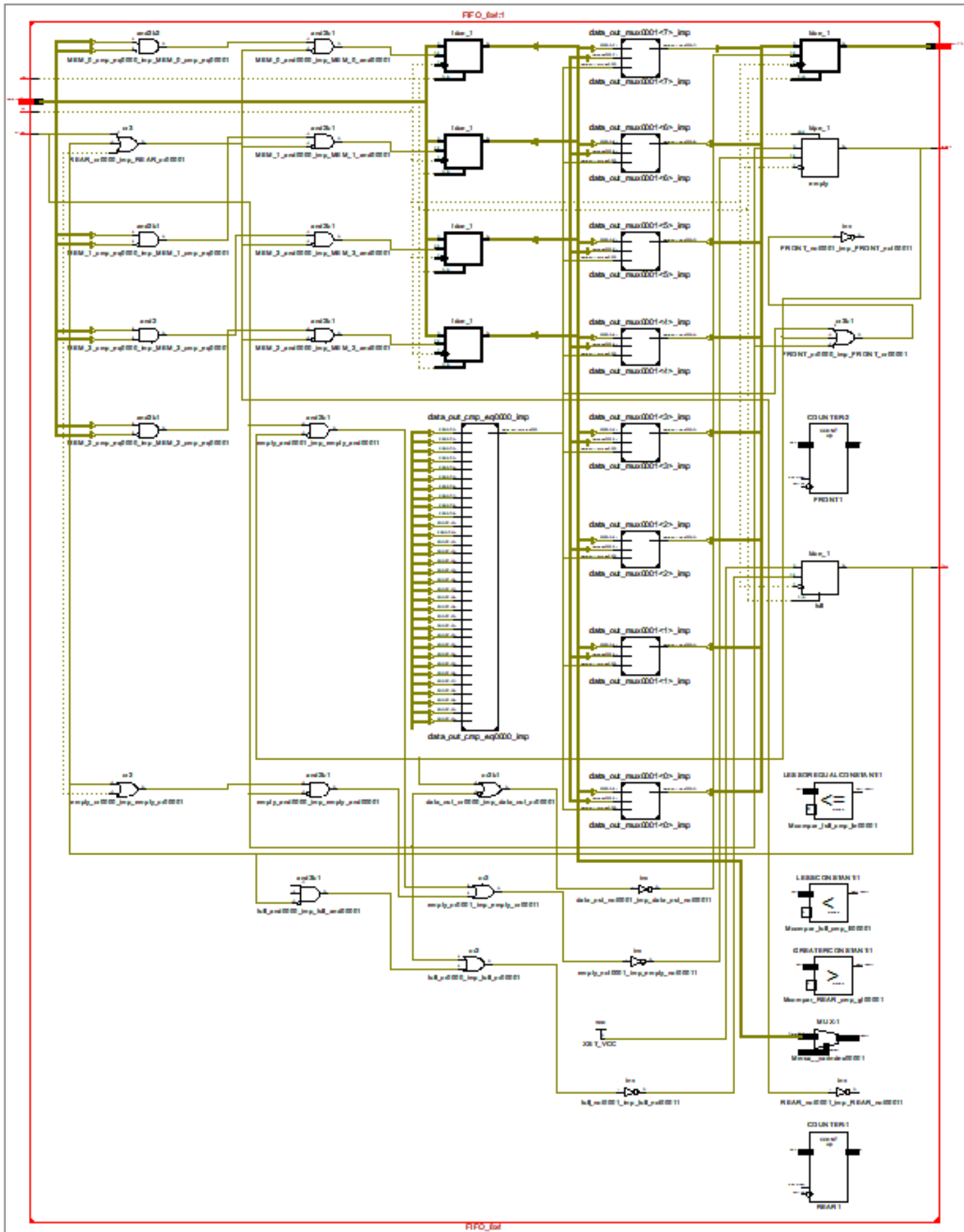

TECHNOLOGY SCHEMATIC

 

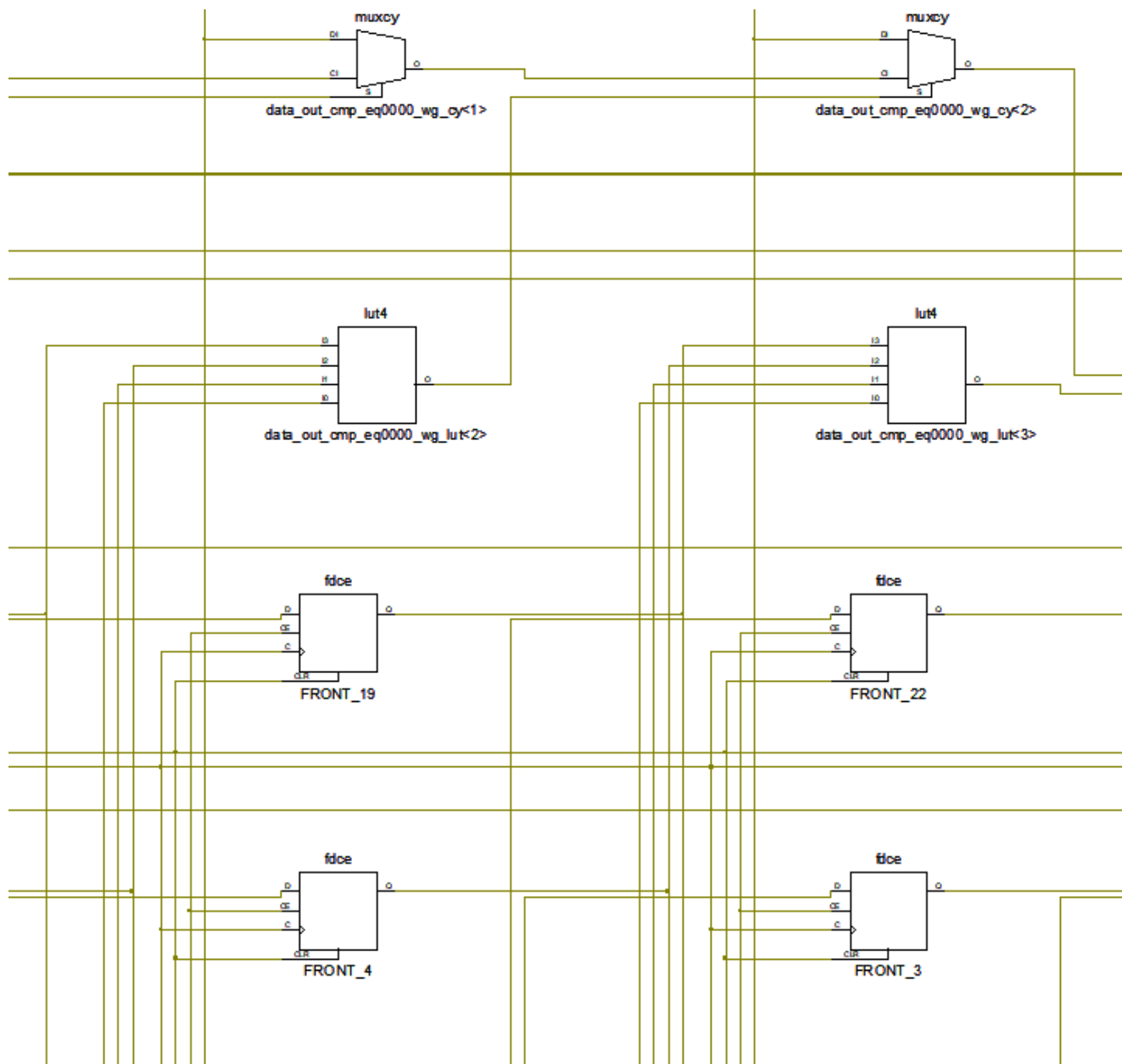

SYNTHESIS REPORT

1) Device Utilisation Summary

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : FIFO_4x8.ngf
Top Level Output File Name : FIFO_4x8
Output Format : NGC
Optimization Goal : Speed
Keep Hierarchy : No
Design Statistics
IOs : 21

Cell Usage :

BELS : 289
GND : 1
INV : 7
LUT1 : 62
LUT2 : 2
LUT2_D : 1
LUT3 : 26
LUT4 : 28
MUXCY : 89
MUXF5 : 8
VCC : 1
XORCY : 64
FlipFlops/Latches : 106
FDCE : 64
FDCE_1 : 41
FDPE_1 : 1
Clock Buffers : 1
BUFGP : 1
IO Buffers : 20
IBUF : 10
OBUF : 10

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	81 out of 2448	3%
Number of Slice Flip Flops:	106 out of 4896	2%
Number of 4 input LUTs:	126 out of 4896	2%
Number of IOs:	21	
Number of bonded IOBs:	21 out of 158	13%
Number of GCLKs:	1 out of 24	4%

Partition Resource Summary:

No Partitions were found in this design.

2) TIMING REPORT

Timing Summary:

Speed Grade: -5

Minimum period: 5.693ns (Maximum Frequency: 175.653MHz)

Minimum input arrival time before clock: 4.609ns

Maximum output required time after clock: 4.221ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM

```
LIBRARY ieee;  
USE ieee.std_logic_1164.ALL;
```

```
ENTITY FIFO_4x8_tb IS  
END FIFO_4x8_tb;
```

```
ARCHITECTURE behavior OF FIFO_4x8_tb IS
```

```
    COMPONENT FIFO_4x8
```

```
    PORT(
```

```
        data_in : IN std_logic_vector(7 downto 0);  
        rst : IN std_logic;  
        clk : IN std_logic;  
        wr_en : IN std_logic;  
        data_out : OUT std_logic_vector(7 downto 0);  
        empty : INOUT std_logic;  
        full : INOUT std_logic  
    );
```

```
END COMPONENT;
```

```
signal data_in : std_logic_vector(7 downto 0) := (others => '0');  
signal rst : std_logic := '1';  
signal clk : std_logic := '0';  
signal wr_en : std_logic := '0';
```

```
signal empty : std_logic;  
signal full : std_logic;
```

```
signal data_out : std_logic_vector(7 downto 0);
```

```
constant clk_period : time := 10 ns;
```

```
BEGIN
```

```
    uut: FIFO_4x8 PORT MAP (  
        data_in => data_in,  
        rst => rst,  
        clk => clk,  
        wr_en => wr_en,  
        data_out => data_out,  
        empty => empty,  
        full => full  
    );
```


```
clk_process :process
begin
    clk <= '0';
    wait for clk_period/2;
    clk <= '1';
    wait for clk_period/2;
end process;

stim_proc_data_in: process
begin
    data_in<=X"01";
    wait for 11 ns;
    data_in<=X"02";
    wait for 10 ns;
    data_in<=X"03";
    wait for 10 ns;
    data_in<=X"04";
    wait for 10 ns;
end process;

stim_proc_rst: process
begin
    rst<='0';
    wait for 90 ns;
    rst<='1';
    wait for 5 ns;
end process;

stim_proc_wr_en: process
begin
    wr_en<='0';
    wait for 50 ns;
    wr_en<='1';
    wait for 40 ns;
end process;
END;
```

ISIM WAVEFORMS

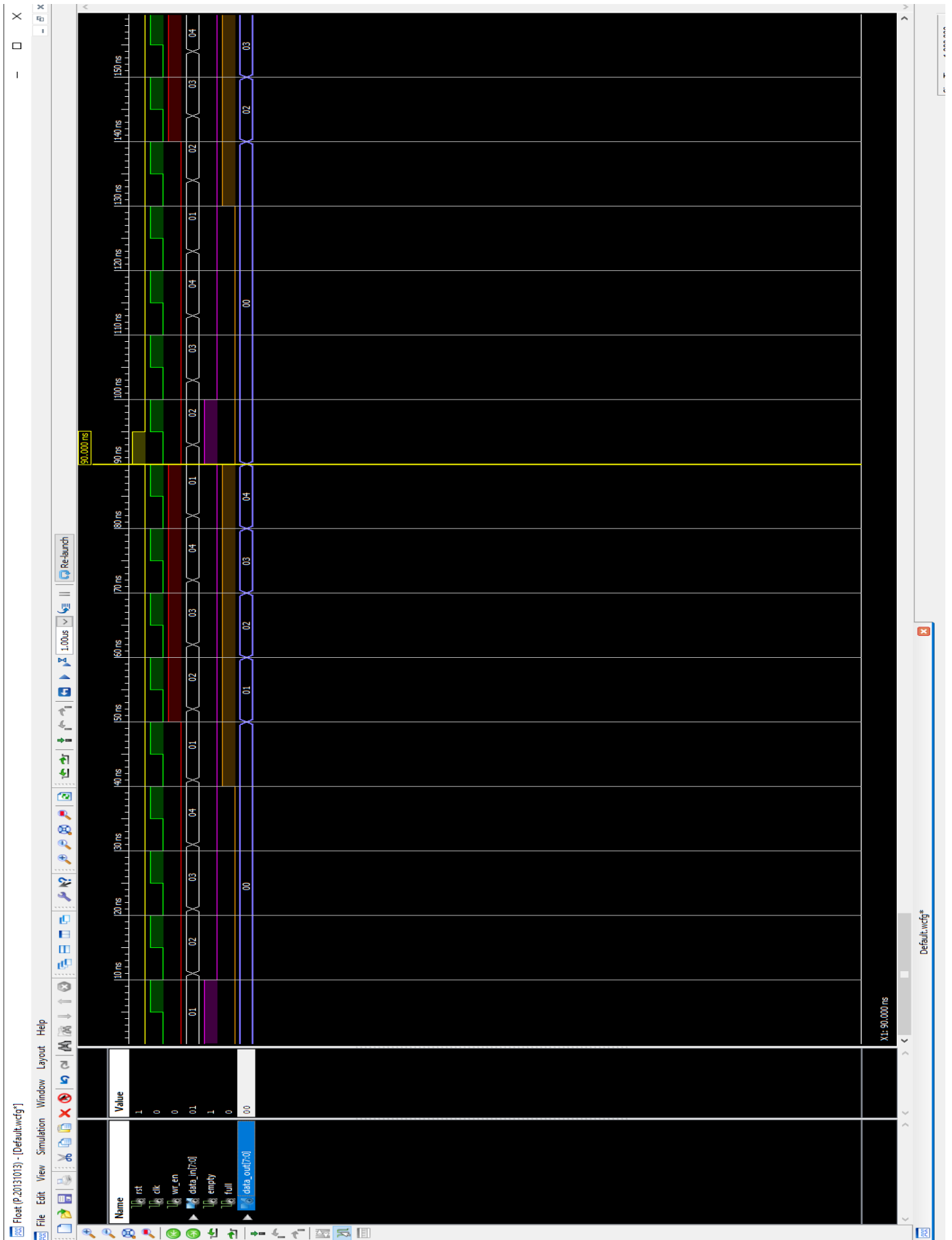

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

NET "data_in[7]" LOC = P165; #sw4-0

NET "data_in[6]" LOC = P167; #sw4-1

NET "data_in[5]" LOC = P163; #sw4-2

NET "data_in[4]" LOC = P164;

NET "data_in[3]" LOC = P161;

NET "data_in[2]" LOC = P162;

NET "data_in[1]" LOC = P160;

NET "data_in[0]" LOC = P153; #sw4-7

NET "data_out[7]" LOC = P179; #sw3-0

NET "data_out[6]" LOC = P180; #sw3-1

NET "data_out[5]" LOC = P177;

NET "data_out[4]" LOC = P178;

NET "data_out[3]" LOC = P152;

NET "data_out[2]" LOC = P168;

NET "data_out[1]" LOC = P171;

NET "data_out[0]" LOC = P172; #sw3-7

NET "clk" LOC = P132;

NET "rst" LOC = P204; #k0

NET "enr" LOC = P184; #sw2-6

NET "enw" LOC = P194; #sw2-7

NET "empty" LOC = P199; #sw1-6

NET "full" LOC = P196; #sw1-7

Conclusion:

Thus we have :

- 1) Modeled a 4x8 FIFO using Behavioral Modeling Style.
- 2) Observed following Schematics: **RTL & Technology Schematics** generated **Post-Synthesis**.
- 3) Interpreted **Device Utilization Summary** in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
- 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
- 5) Written a TESTBENCH to verify the functionality of 4x8 FIFO & verified the functionality as per the TRUTH-TABLE by observing ISIM Waveforms.
- 6) Used PlanAhead Editor for pin-locking.
- 7) Prototyped the FPGA **XC3S250EPQ208-5** to realize 4x8 FIFO & verified its operation by giving suitable input combinations.