 


## TITLE PAGE

Class	:	BE - 8
Roll. No	:	42428
Assignment No.	:	B. 2
Assignment Name	:	2:1 MUX using TG
Date Of Performance	:	21-11-2020

**Theory:**


### Schematic of TG-



For  $C=1$  ,  $O|P=I|P$   
 $C=0$  ,  $O|P=0$

### Schematic of 2:1 MUX using TG


Symbol of TG

 

### Truth Table


C	O/P
1	I/P
0	0

Symbol of 2:1 MUX

 

### Truth Table

S	$Y_{MUX}$
0	$I_0$
1	$I_1$

 


All PMOS & NMOS Devices have sizes-

$$P = n = \left( \frac{500}{100} \right) \text{nm} = 5$$


$$P/n = 1$$

## LAYOUT

### a) Transmission Gate

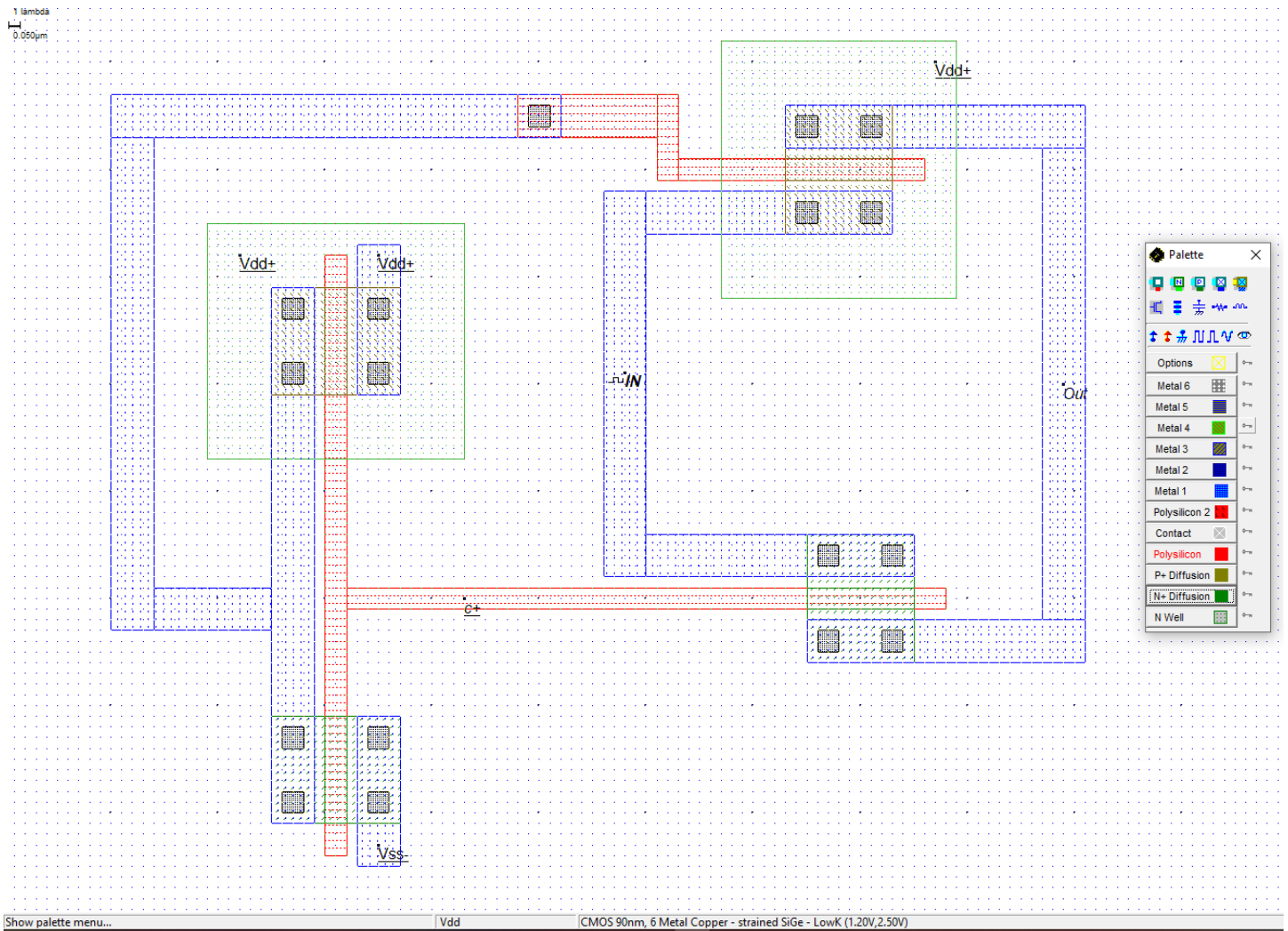


## b) 2:1 MUX using 2 Transmission Gates

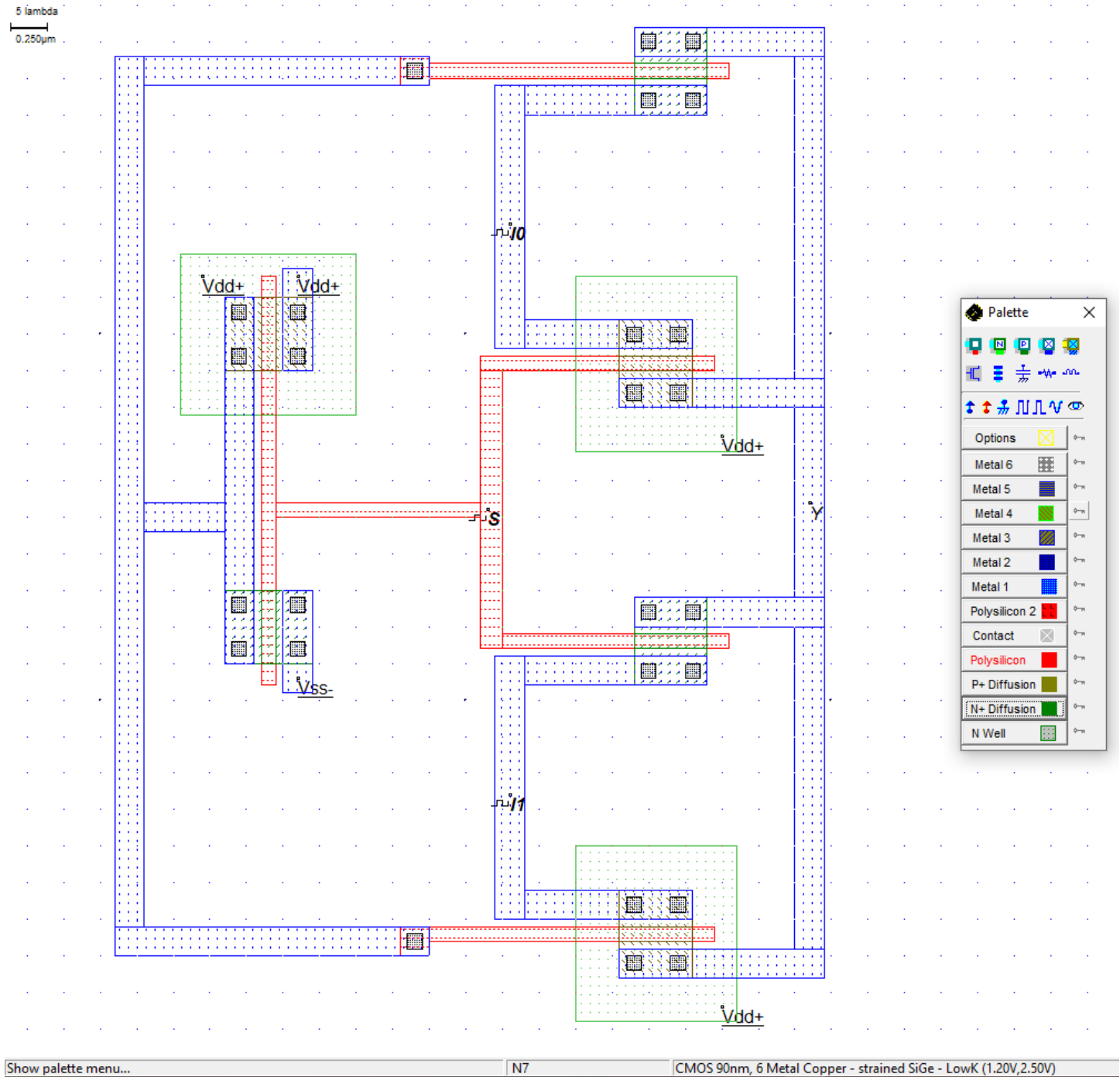


## Waveforms

 
### a) Output of Transmission Gate when $c = 1$


 
### b) Output of Transmission Gate when $c = 0$



### c) Output of 2:1 MUX

 

**Conclusion:**

**Thus we have :**

- 1) Drawn the LAYOUT for Transmission Gate using 90 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 3) Using the above verified LAYOUT of Transmission gate, drawn the LAYOUT for 2:1 MUX.
- 4) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 5) TG is a CMOS Switch; hence it gives both STRONG-1 and STRONG-0 at the output.
- 6) Multiplexer is built using 2 TG Switches and 1 CMOS Inverter hence, it is a CMOS Multiplexer, gives both STRONG-1 and STRONG-0 at the output.
- 7) TG Logic reduces the transistor count for MUX implementation over CMOS Logic from 20 to 6.