 


## TITLE PAGE

Class	:	BE – 8
Roll. No	:	42428
Assignment No.	:	B. 1a
Assignment Name	:	CMOS Inverter and Analysis
Date Of Performance	:	03-11-2020 & 21-11-2020

## Theory:

### Symbol.



### Truth Table


$V_{IN}$	$V_{OUT} = \overline{V_{IN}}$
0	STRONG-1
1	STRONG-0

O/p	Value of $V_{OUT}$ (V)
1) STRONG-1	$+V_{DD}$
2) WEAK-1	$< +V_{DD}$
3) STRONG-0	$-V_{SS} (0)$
4) WEAK-0	$> 0$



$$P_{dyn} = C_L (V_{DD})^2 f$$

$\rightarrow P_{dyn} \propto C_L$   
 $\rightarrow P_{dyn} \propto (V_{DD})^2$   
 $\rightarrow P_{dyn} \propto f$

For 90nm Foundry  
 $V_{DD} = +1.2V$

 

### Schematics

  

$$P = \frac{W_p}{L_p} = \left( \frac{500}{100} \right) \text{nm} = 5$$

$$n = \frac{W_n}{L_n} = \left( \frac{500}{100} \right) \text{nm} = 5$$

$$\frac{P}{n} = 1$$

Nominal values-

$$C_L = 0.01 \text{ pF}$$

$$f = 2.5 \text{ GHz}$$

$$C_L' = 0.005 \text{ pF}$$

$$C_L'' = 0.02 \text{ pF}$$

$$f' = 1.25 \text{ GHz}$$

$$f'' = 5 \text{ GHz}$$

$$P = \frac{W_p}{L_p} = \left( \frac{1000}{200} \right) \text{nm} = 5$$

$$n = \frac{W_n}{L_n} = \left( \frac{1000}{200} \right) \text{nm} = 5$$

$$\frac{P}{n} = 1$$

Nominal Values


$$C_L = 0.01 \text{ pF}$$

$$f = 2.5 \text{ GHz}$$

$C_L$  &  $f$  are not varied.



## LAYOUT

### a) CMOS Inverter with 90 nm Foundry

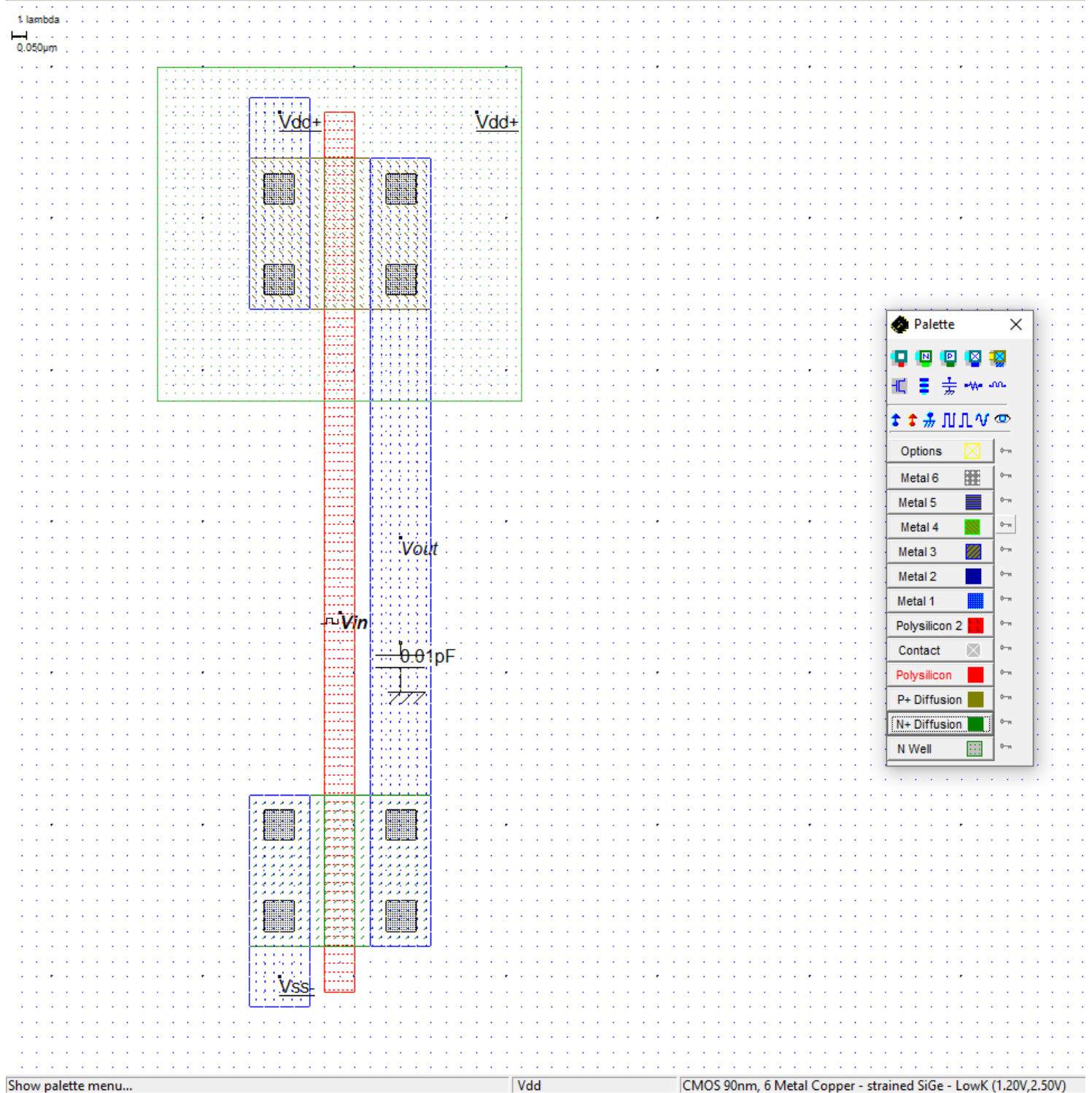


## b) CMOS Inverter with 180 nm Foundry

1 lambda  
0.180um

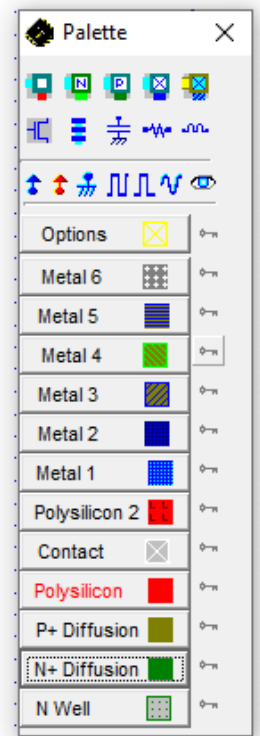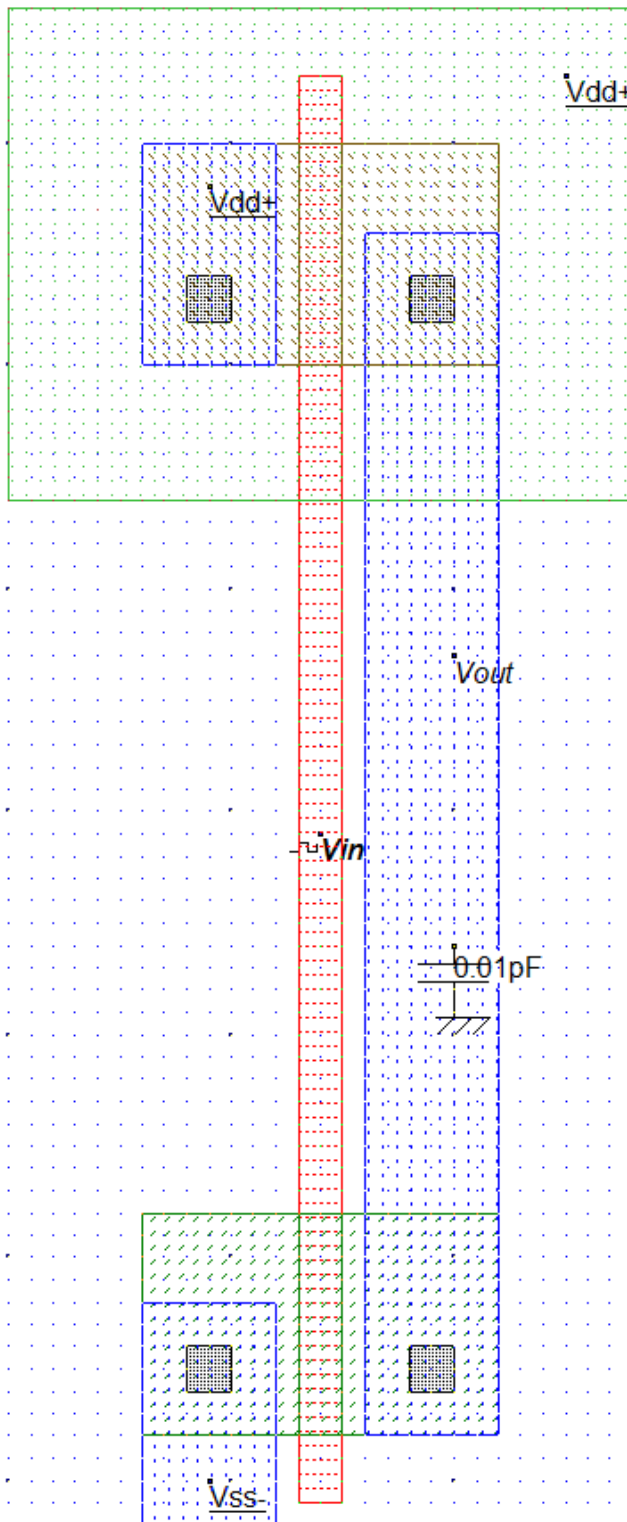


## Waveforms


a)  $V_{in}$  ,  $V_{out}$

 


## b) Vout , Iout

 

 **c)  $f_{\text{clk}} = 1.25 \text{ GHz}$  ,  $C_L = 0.01 \text{ pF}$  ,  $V_{DD} = 1.2 \text{ V}$**




 **d)  $f_{\text{clk}} = 2.5 \text{ GHz}$  ,  $C_L = 0.01 \text{ pF}$  ,  $V_{DD} = 1.2 \text{ V}$**






 
e)  $f_{\text{clk}} = 5 \text{ GHz}$ ,  $C_L = 0.01 \text{ pF}$ ,  $V_{DD} = 1.2 \text{ V}$



 
**f)  $f_{\text{clk}} = 2.5 \text{ GHz}$  ,  $C_L = 0.005 \text{ pF}$  ,  $V_{DD} = 1.2 \text{ V}$**



 **g)  $f_{\text{clk}} = 2.5 \text{ GHz}$ ,  $C_L = 0.02 \text{ pF}$ ,  $V_{DD} = 1.2 \text{ V}$**



 **h)  $f_{\text{clk}} = 2.5 \text{ GHz}$ ,  $C_L = 0.01 \text{ pF}$ ,  $V_{DD} = 2 \text{ V}$**



PERFORMANCE ANALYSIS

OT-1 :-  $f_{clk} = 2.5 \text{ GHz}$  ,  $V_{dd} = 1.2 \text{ V}$  (90 nm)

$C_L$ (pF)	$P_{dyn}$ ( $\mu\text{W}$ )
0.005	20.759
0.01	38.025
0.02	71.913

OT-2 :-  $C_L = 0.01 \text{ pF}$  ,  $V_{dd} = 1.2 \text{ V}$  (90 nm)

$f_{clk}$ (GHz)	$P_{dyn}$ ( $\mu\text{W}$ )
1.25	21.279
2.5	38.025
5	65.701

OT-3 :-  $f_{clk} = 2.5 \text{ GHz}$  ,  $C_L = 0.01 \text{ pF}$

$V_{dd}$ (V)	$P_{dyn}$ ( $\mu\text{W}$ )
1.2	38.025
2	108

$$\frac{P_{dyn2}}{P_{dyn1}} = \left[ \frac{V_{dd2}}{V_{dd1}} \right]^2 = \left[ \frac{2}{1.2} \right]^2 = 2.78$$

## **Conclusion:**

**Thus we have :**

- 1) Drawn the LAYOUT for CMOS Inverter using 90 nm & 180 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 3) Noted the values of  $P_{dynamic}$  for floating Load.
- 4) Appreciated the validity of the mathematical model :  $P_{dynamic} = C_L * (V_{dd})^2 * f_{clk}$  ; by Doubling & Halving the values of  $C_L$  &  $f_{clk}$
- 5) Found a reduction in  $P_{dynamic}$  by using a better Foundry i.e. 90 nm instead of 180 nm.
- 6) Learnt that the presence of spikes in O/P waveform at Switching instants indicate the inability of the MOSFETs to switch at GHz frequencies.
- 7) Learnt that the using a better Foundry enables the MOSFETs the inability of the MOSFETS to switch at Higher GHz frequencies, as proved by the removal of Spikes at the O/P.